

4. The equivalent capacitance is

$$C_{\text{eq}} = C_3 + \frac{C_1 C_2}{C_1 + C_2} = 4.00 \mu\text{F} + \frac{(10.0 \mu\text{F})(8.00 \mu\text{F})}{10.0 \mu\text{F} + 8.00 \mu\text{F}} = 8.44 \mu\text{F}.$$

6. (a) The charge  $q_3$  in the figure is  $q_3 = C_3V = (2.00 \mu\text{F})(100 \text{ V}) = 2.00 \times 10^{-4} \text{ C}$ .

(b)  $V_3 = V = 100 \text{ V}$ .

(c) Using  $U_i = \frac{1}{2}C_iV_i^2$ , we have  $U_3 = \frac{1}{2}C_3V_3^2 = 1.00 \times 10^{-2} \text{ J}$ .

(d) From the figure,

$$q_1 = q_2 = \frac{C_1C_2V}{C_1 + C_2} = \frac{(10.0 \mu\text{F})(5.00 \mu\text{F})(100 \text{ V})}{10.0 \mu\text{F} + 5.00 \mu\text{F}} = 3.33 \times 10^{-4} \text{ C}.$$

(e)  $V_1 = q_1/C_1 = 3.33 \times 10^{-4} \text{ C}/10.0 \mu\text{F} = 33.3 \text{ V}$ .

(f)  $U_1 = \frac{1}{2}C_1V_1^2 = 5.55 \times 10^{-3} \text{ J}$ .

(g) From part (d), we have  $q_2 = q_1 = 3.33 \times 10^{-4} \text{ C}$ .

(h)  $V_2 = V - V_1 = 100 \text{ V} - 33.3 \text{ V} = 66.7 \text{ V}$ .

(i)  $U_2 = \frac{1}{2}C_2V_2^2 = 1.11 \times 10^{-2} \text{ J}$ .

14. Each capacitor has 12.0 V across it, so Eq. 25-1 yields the charge values once we know  $C_1$  and  $C_2$ . From Eq. 25-9,

$$C_2 = \frac{\epsilon_0 A}{d} = 2.21 \times 10^{-11} \text{ F} ,$$

and from Eq. 25-27,

$$C_1 = \frac{\kappa \epsilon_0 A}{d} = 6.64 \times 10^{-11} \text{ F} .$$

This leads to

$$q_1 = C_1 V_1 = 6.64 \times 10^{-10} \text{ C}, \quad q_2 = C_2 V_2 = 2.21 \times 10^{-10} \text{ C}.$$

The addition of these gives the desired result:  $q_{\text{tot}} = 8.85 \times 10^{-10} \text{ C}$ . Alternatively, the circuit could be reduced to find the  $q_{\text{tot}}$ .

16. (a) We use Eq. 25-14:

$$C = 2\pi\epsilon_0\kappa \frac{L}{\ln(b/a)} = \frac{(4.7)(0.10 \text{ m})}{2\left(8.99 \times 10^9 \frac{\text{N}\cdot\text{m}^2}{\text{C}^2}\right)\ln(3.8 \text{ cm}/3.6 \text{ cm})} = 0.48 \text{ nF}.$$

(b) The breakdown potential is  $(14 \text{ kV/mm})(3.8 \text{ cm} - 3.6 \text{ cm}) = 28 \text{ kV}$ .

20. (a) We calculate the charged surface area of the cylindrical volume as follows:

$$A = 2\pi rh + \pi r^2 = 2\pi(0.20 \text{ m})(0.10 \text{ m}) + \pi(0.20 \text{ m})^2 = 0.25 \text{ m}^2$$

where we note from the figure that although the bottom is charged, the top is not. Therefore, the charge is  $q = \sigma A = -0.50 \mu\text{C}$  on the exterior surface, and consequently (according to the assumptions in the problem) that same charge  $q$  is induced in the interior of the fluid.

(b) By Eq. 25-21, the energy stored is

$$U = \frac{q^2}{2C} = \frac{(5.0 \times 10^{-7} \text{ C})^2}{2(50 \times 10^{-12} \text{ F})} = 2.5 \times 10^{-3} \text{ J}.$$

(c) Our result is within a factor of 4 of that needed to cause a spark. Our conclusion is that it will probably not cause a spark; however, there is not enough of a safety factor to be sure.

39. **THINK** After the switches are closed, the potential differences across the capacitors are the same and they are connected in parallel.

**EXPRESS** The potential difference from  $a$  to  $b$  is given by  $V_{ab} = Q/C_{\text{eq}}$ , where  $Q$  is the net charge on the combination and  $C_{\text{eq}}$  is the equivalent capacitance.

**ANALYZE** (a) The equivalent capacitance is  $C_{\text{eq}} = C_1 + C_2 = 4.0 \times 10^{-6}$  F. The total charge on the combination is the net charge on either pair of connected plates. The initial charge on capacitor 1 is

$$q_1 = C_1 V = (1.0 \times 10^{-6} \text{ F})(200 \text{ V}) = 2.0 \times 10^{-4} \text{ C}$$

and the initial charge on capacitor 2 is  $q_2 = C_2 V = (3.0 \times 10^{-6} \text{ F})(200 \text{ V}) = 6.0 \times 10^{-4} \text{ C}$ . With opposite polarities, the net charge on the combination is

$$Q = 6.0 \times 10^{-4} \text{ C} - 2.0 \times 10^{-4} \text{ C} = 4.0 \times 10^{-4} \text{ C}.$$

The potential difference is

$$V_{ab} = \frac{Q}{C_{\text{eq}}} = \frac{4.0 \times 10^{-4} \text{ C}}{4.0 \times 10^{-6} \text{ F}} = 100 \text{ V}.$$

(b) The charge on capacitor 1 is now  $q'_1 = C_1 V_{ab} = (1.0 \times 10^{-6} \text{ F})(100 \text{ V}) = 1.0 \times 10^{-4} \text{ C}$ .

(c) The charge on capacitor 2 is now  $q'_2 = C_2 V_{ab} = (3.0 \times 10^{-6} \text{ F})(100 \text{ V}) = 3.0 \times 10^{-4} \text{ C}$ .

**LEARN** The potential difference  $V_{ab} = 100 \text{ V}$  is half of the original  $V = 200 \text{ V}$ , so the final charges on the capacitors are also halved.